 


## Lab 7: VHDL 16-Bit Shifter


**Objectives :**

Design a 16-bit shifter which need implement eight shift operations: logic shift right, logic shift left, arithmetic shift right, arithmetic shift left, rotate right, rotate left rotate left with carry, rotate left with carry.

**16-Bit Shifter specification:**



**Figure 1. Symbol**

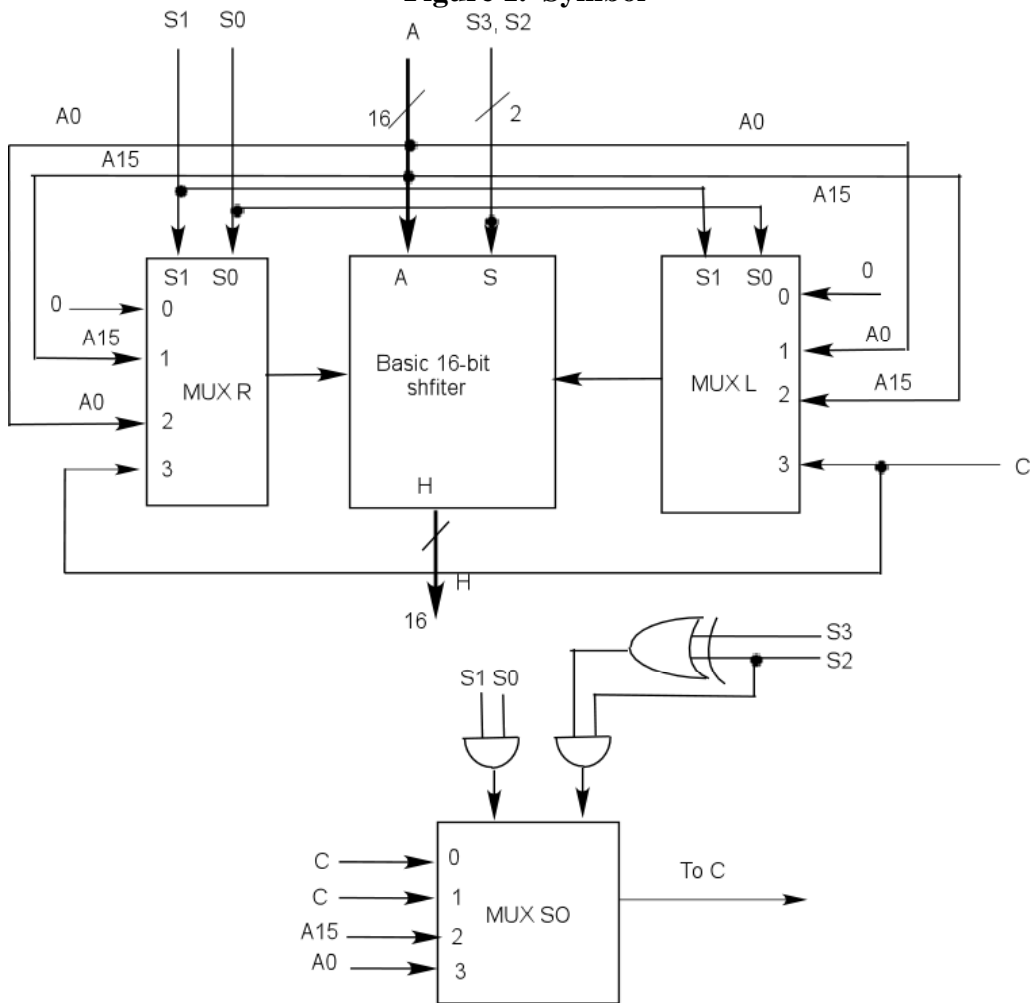

**Figure 2. Logic diagram**

S <sub>1</sub>	S <sub>0</sub>	Shift Operation
0	0	Logic Shift
0	1	Arithmetic shift
1	0	Rotate
1	1	Rotate with carry

S <sub>3</sub>	S <sub>2</sub>	Shift direction
0	0	Parallel Load
0	1	Shift Right with I <sub>L</sub>
1	0	Shift Left with I <sub>R</sub>
1	1	No Change

In the above logic diagram, for the unit “16-bit basic shifter” design you may refer to the available code for the Universal Shift Register with parallel load(three different style codes are given).

### Universal Shifter Register with parallel Load

 


Figure 3. Universal Shift Register Symbol

S <sub>1</sub>	S <sub>0</sub>	Next State after rising_edge of clk	Description
0	0	Q[3..0] <= Q[3..0]	No Change
0	1	Q[3..0] <= I[3..0]	Parallel Load
1	0	Q[3..1] <= Q[2..0], Q[0] <= I <sub>R</sub>	Shift Left with I <sub>R</sub>
1	1	Q[3] <= I <sub>L</sub> , Q[2..0] <= Q[3..1]	Shift Right with I <sub>L</sub>

#### 1. Universal shift register using array slicing and concatenation method.

LISTING 1: Save as Filename="univ\_shiftreg1.vhd"

```

LIBRARY IEEE;
USE IEEE.STD_LOGIC_1164.ALL;
USE IEEE.STD_LOGIC_UNSIGNED.ALL;
USE IEEE.NUMERIC_BIT.ALL;

```

```

ENTITY univ_shiftreg1 IS
    PORT(clk, il, ir : IN BIT;
         s: IN BIT_VECTOR(1 DOWNT0 0);
         i : IN BIT_VECTOR(3 DOWNT0 0);
         q : OUT BIT_VECTOR(3 DOWNT0 0));
END univ_shiftreg1;

ARCHITECTURE beh1 OF univ_shiftreg1 IS
    SIGNAL qtmp : BIT_VECTOR(3 DOWNT0 0);
BEGIN
    PROCESS(clk)
    BEGIN

        IF (clk = '1' AND clk'EVENT) THEN
            CASE s IS
                WHEN "00" => qtmp <= qtmp;
                WHEN "01" => qtmp <= i;
                WHEN "10" => qtmp<=qtmp(2 DOWNT0 0) & ir;
                WHEN "11" => qtmp<=il & qtmp(3 DOWNT0 1);
                WHEN OTHERS => NULL;
            END CASE;
        END IF;
    END PROCESS;
    q <= qtmp;
END beh1;

```

## 2. Universal shift register using shifting operators: sll, srl.

LISTING 2: Save as Filename="univ\_shiftreg2.vhd"

```

library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_bit.all;

entity univ_shiftreg2 is
    port(clk,il,ir :in bit;
         s :in bit_vector(1 downto 0);
         i : in bit_vector(3 downto 0);
         q : out bit_vector(3 downto 0));

end univ_shiftreg2;

architecture beh2 of univ_shiftreg2 is

    signal qtmp: bit_vector(5 downto 0);

begin
    process(clk)
    begin
        if (clk = '1' and clk'event) then
            case s is
                when "00" =>
                    qtmp <= qtmp;

```

```

when "01" =>
qtmp <=il&i&ir;
when "10" =>
qtmp <= (il&qtmp(4 downto 1)&ir) sll 1;

when "11" =>
qtmp<= (il&qtmp(4 downto 1)&ir) srl 1;


when others =>
null;
end case;
end if;

end process;
q<=qtmp(4 downto 1);

end beh2;

```

**3. Universal shift register using structural modelling.**

 

**Figure 4. Universal Shift Register Implementation.**

MUX_sel	NEXT STATE after rising_edge of clk				Operation
S1S0	Q3	Q2	Q1	Q0	
00	Q3	Q2	Q1	Q0	No Change
01	I3	I2	I1	I0	Parallel Load
10	Q2	Q1	Q0	IR	Shift left
11	IL	Q3	Q2	Q1	Shift right

**Write a vhdl code to model (entity and architecture) a four to one multiplexer called “MUX41”.**

**LISTING 3: Save as Filename=“univ\_shiftreg3.vhd”**

```

LIBRARY IEEE;
USE IEEE.STD_LOGIC_1164.ALL;
ENTITY MUX41 IS
PORT (i3, i2, i1, i0 : IN BIT;

```

```

        s: IN BIT_VECTOR(1 DOWNTO 0);
        o: OUT BIT);
END MUX41;
ARCHITECTURE arch_mux41 OF MUX41 IS
BEGIN
    PROCESS(i3, i2, i1, i0, s)
    BEGIN
        CASE s IS
            WHEN "00" => o <= i0;
            WHEN "01" => o <= i1;
            WHEN "10" => o <= i2;
            WHEN "11" => o <= i3;
            WHEN OTHERS => NULL;
        END CASE;
    END PROCESS;
END arch_mux41

```

**Write a vhdl code to model (entity and architecture) d flip-flop called “DFF”.**

```

LIBRARY IEEE;
USE IEEE.STD_LOGIC_1164.ALL;
ENTITY DFF IS
    PORT(d, clk : IN BIT;
         q, qb : OUT BIT);
END DFF;
ARCHITECTURE arch_dff OF DFF IS
BEGIN
    PROCESS(clk)
        VARIABLE q_temp : BIT;
    BEGIN
        IF(clk'EVENT AND clk='1')THEN
            q_temp := d;
        END IF;
        q <= q_temp;
        qb <= NOT q_temp;
    END PROCESS;
END arch_dff;

```

**Using DFF and MUX41 components, generates the structural model of the “univ\_shiftreg”. That is, show the port map for each of the components shown in Fig 2.**

```

LIBRARY IEEE;
USE IEEE.STD_LOGIC_1164.ALL;
ENTITY univ_shiftreg3 IS
    PORT(clk, il, ir : IN BIT;
         s: IN BIT_VECTOR(1 DOWNTO 0);
         i : IN BIT_VECTOR(3 DOWNTO 0);
         q : OUT BIT_VECTOR(3 DOWNTO 0));
END univ_shiftreg3;
ARCHITECTURE struct OF univ_shiftreg3 IS
COMPONENT MUX41
    PORT (i3, i2, i1, i0 : IN BIT;
         s: IN BIT_VECTOR(1 DOWNTO 0);
         o: OUT BIT);
END COMPONENT;
COMPONENT DFF
    PORT(d, clk : IN BIT;

```

```

        q, qb : OUT BIT);
END COMPONENT;
FOR U1, U2, U3, U4: MUX41 USE ENTITY WORK.MUX41(arch_mux41);
FOR U5, U6, U7, U8: DFF USE ENTITY WORK.DFF(arch_dff);

    SIGNAL o: BIT_VECTOR(3 DOWNTO 0);
    SIGNAL qb: BIT_VECTOR(3 DOWNTO 0);
    SIGNAL qt:BIT_VECTOR(3 DOWNTO 0);
BEGIN
    U1:MUX41 PORT MAP(il,qt(2), i(3), qt(3), s, o(3));
    U2:MUX41 PORT MAP(qt(3), qt(1), i(2), qt(2), s, o(2));
    U3:MUX41 PORT MAP(qt(2), qt(0), i(1), qt(1), s, o(1));
    U4:MUX41 PORT MAP(qt(1), ir, i(0), qt(0), s, o(0));
    U5:DFF PORT MAP(o(3), clk, qt(3), qb(3));
    U6:DFF PORT MAP(o(2), clk, qt(2), qb(2));
    U7:DFF PORT MAP(o(1), clk, qt(1), qb(1));
    U8:DFF PORT MAP(o(0), clk, qt(0), qb(0));
    q <= qt;
END struct;

```

---

### Combinatorial Implementation of Basic 4-bit Shifter\*

A combinatorial implementation of basic 4 bit shifter is given in Fig 5. Please expand it to 16 bit shifter and use it in the implementation of Figure 2 instead of universal shift register. (S is 2 bit selection signal,  $S = S_1S_0$ )

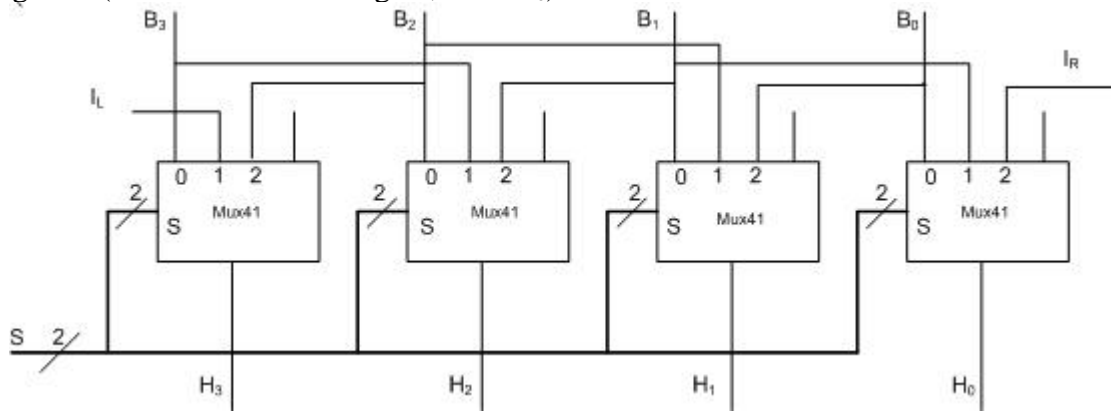


Figure 5. 4 bit shifter

**\*NOTE: This is 4-bit shifter implementation to be used in the project**